

Course Title:	
Course Number:	
Semester/Year (e.g.F2016)	

Instructor:	
--------------------	--

<i>Assignment/Lab Number:</i>	
<i>Assignment/Lab Title:</i>	

<i>Submission Date:</i>	
<i>Due Date:</i>	

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*

*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

ELE 734: Prelab 3

Q1. assume $T_{pdf} = k \cdot T_{pdr}$ $\frac{T_{pdf}}{T_{pdr}} = k$

i) high skewed $\rightarrow T_{pdf} = 1.5 \cdot T_{pdr}$

$$\frac{T_{pdf}}{T_{pdr}} = 1.5$$

$$k = 1.5 = 3/2$$

ii) unskewed $\rightarrow T_{pdf} = T_{pdr}$

$$\frac{T_{pdf}}{T_{pdr}} = 1$$




$$k = 1$$

iii) low skewed $\rightarrow 1.5 T_{pdf} = T_{pdr}$

$$\frac{T_{pdf}}{T_{pdr}} = \frac{1}{1.5} = \frac{2}{3}$$



$$k = \frac{2}{3}$$

a) CMOS Inverter sizing

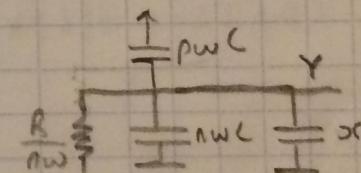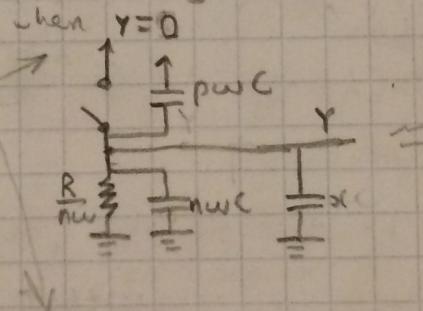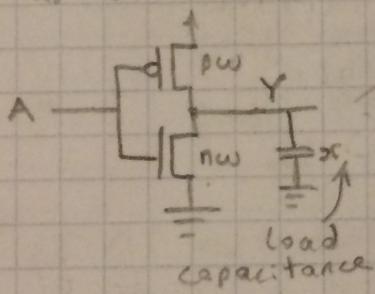

$$T_{pdf} = \frac{R}{nw} (nwC + pwC + x)$$

when $y=1$

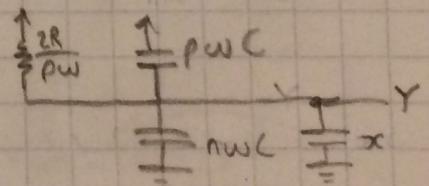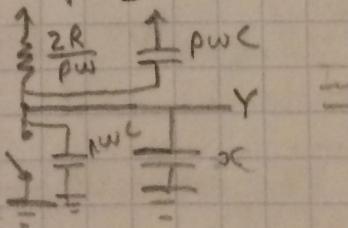

$$T_{pdr} = \frac{2R}{pw} (nwC + pwC + x)$$

$$T_{pdf} = k \cdot T_{pdr}$$

$$\frac{R}{nw} (nwC + pwC + x) = k \cdot \frac{2R}{pw} (nwC + pwC + x)$$

$$\frac{1}{n} = k \cdot \frac{2}{p}$$

$$\frac{p}{n} = \frac{2k}{1}$$

$$\begin{array}{|c|} \hline p = 2k \\ n = 1 \\ \hline \end{array}$$

assuming $\alpha = 50FF$ when $T_p = 100 \text{ ps}$. and $K=1$

$$T_p = \frac{T_{pd3} + T_{pdr}}{2} = \frac{T_{pdr} + T_{pd3}}{2} = T_{pdr}$$

$$T_p = \frac{2R}{\rho w} (nwC + pwC + \alpha)$$

$$T_p = \frac{2R}{(2)w} ((1)wC + (2)wC + \alpha)$$

$$T_p = \frac{R}{w} (3wC + \alpha) \rightarrow w \left(\frac{T_p}{R} - 3C \right) = \alpha$$

$$\frac{w T_p}{R} = 3wC + \alpha \quad \alpha = \frac{\alpha}{\frac{T_p}{R} - 3C} = \frac{(50FF)}{\frac{(100ps)}{(R/2)10k\Omega} - 3(1fF)}$$

$$\frac{w T_p}{R} - 3wC = \alpha \quad w = 4.375620635 \approx 4.376$$

assume $C \approx C_g \times w = C_g \cdot n \approx (1fF/\mu m)(1\mu m) \approx 1fF$, $R = 10k\Omega$


w_1 for
unit nmos

b) NOR2 gate sizing



$$Y = \overline{A+B} \rightarrow \bar{Y} = \overline{(A+B)}$$

$$Y = \overline{A} \cdot \overline{B} \quad \text{PMOS}$$

$$\bar{Y} = A + B \quad \text{NMOS}$$

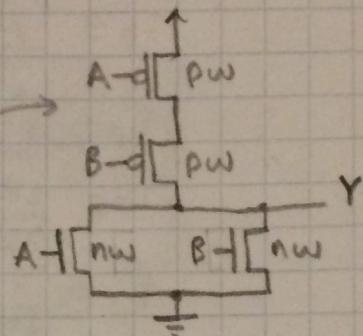


when $Y=1$, worst case delay is:

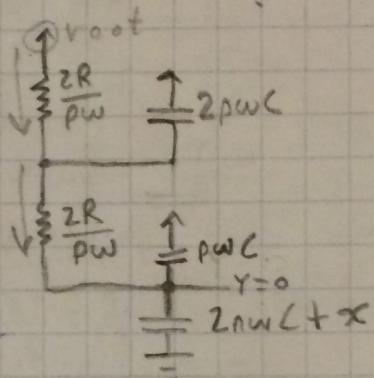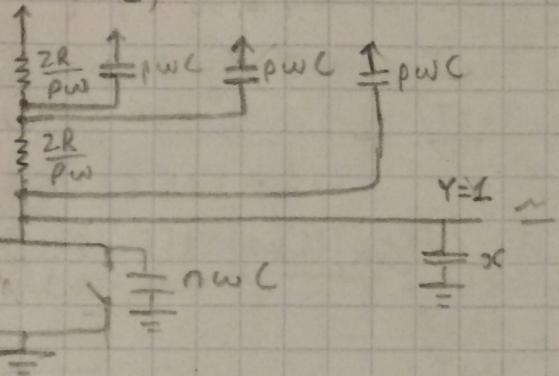

$$T_{pd़f} = \frac{2R}{pw} (2pwC + pwC + 2nwC + x) + \frac{2R}{pw} (pwC + 2nwC + x)$$

$$T_{pd़r} = \frac{2R}{pw} (4nwC + 4pwC + 2x) = \frac{4R}{pw} (2nwC + 2pwC + x)$$

when $Y=0$, worst case delay is:

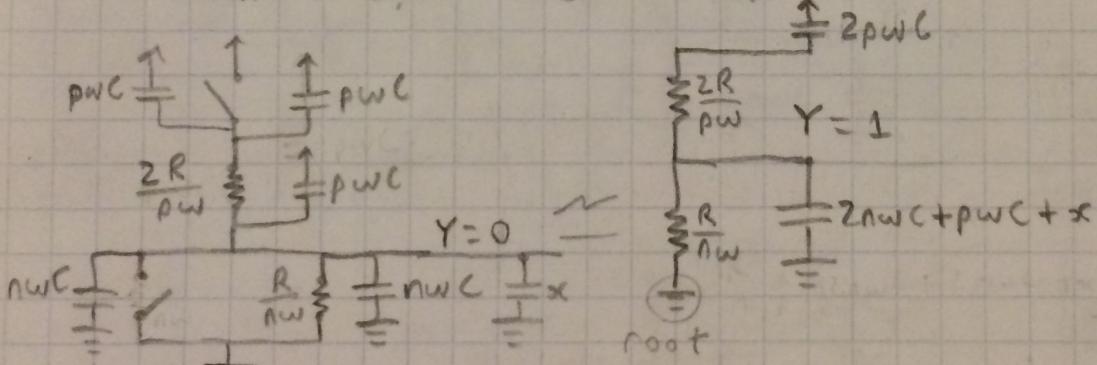

$$T_{pd़f} = \frac{R}{nw} (2nwC + pwC + x + 2pwC) = \frac{R}{nw} (2nwC + 3pwC + x)$$

$$T_{pd़f} = k \cdot T_{pd़r}$$

$$\frac{R}{nw} (2nwC + 3pwC + x) = k \cdot \frac{4R}{pw} (2nwC + 2pwC + x)$$

$$\frac{1}{n} = k \cdot \frac{4}{p}$$

$$\frac{p}{n} = \frac{4k}{1} = \frac{wp}{wn}$$

$$\therefore p = 4k \text{ nm}$$

$n = 1 \text{ nm}$ ← assumes W_n for unit NMOS is 1 μm

when $T_p = 100 \text{ ps}$, assume:

unskewed gate ($k=1$)

$$\alpha = 50 \text{ fF}$$

$$C = C_g \times W_n = C_g \times n = (1 \text{ fF}/\mu\text{m})(1 \mu\text{m}) = 1 \text{ fF}$$

$$W_n = 1 \mu\text{m}$$

$$R = 10 \text{ k}\Omega \cdot \ln(2)$$

$$\frac{P}{T} = \frac{4k}{1} = \frac{4(1)}{1} = 4 \quad T_p = \frac{T_p df + T_p dr}{R} = \frac{\left[\frac{R}{\rho w} (2nwC + 3\rho wC + x) \right] + \left[\frac{4R}{\rho w} (2nwC + 2\rho wC + x) \right]}{R} \\ \rightarrow T_p = \frac{\left[\frac{R}{(1)w} (2(1)wC + 3(4)wC + x) \right] + \left[\frac{4R}{(4)w} (2(1)wC + 2(4)wC + x) \right]}{R}$$

$$T_p = \frac{R}{w} (2wC + 12wC + x) + \frac{R}{w} (2wC + 8wC + x) \quad P = 4(1) = 4$$

$$T_p = \frac{R}{2w} (24wC + 2x)$$

$$T_p = \frac{R}{w} (12wC + x)$$

$$w \frac{T_p}{R} = 12wC + x$$

$$w \frac{T_p}{R} - 12wC = x$$

$$w \left(\frac{T_p}{R} - 12C \right) = x$$

$$w = \frac{x}{\frac{T_p}{R} - 12C}$$

$$w = \frac{(50 \text{ fF})}{\frac{(100 \text{ ps})}{(10 \text{ k}\Omega \cdot \ln 2)} - 12(1 \text{ fF})} = \frac{50}{\frac{10}{\ln(2)} - 12}$$

$$w \approx 20.60198668 \approx 20.602$$

assume, $W_p = p \cdot w = 4 \mu\text{m} \cdot k \cdot w$, $W_n = n \cdot w = 1 \mu\text{m} \cdot w$

i) high skewed nor2 gate ($k=1.5$)

$$W_p = 4 \mu\text{m} (1.5) (20.602) \approx 123.6119201 \mu\text{m} \approx 123.612 \mu\text{m}$$

$$W_n = 1 \mu\text{m} (20.602) \approx 20.602 \mu\text{m}$$

ii) unskewed nor2 gate ($k=1$)

$$W_p = 4 \mu\text{m} (1) (20.602) \approx 82.40794672 \mu\text{m} \approx 82.408 \mu\text{m}$$

$$W_n = 1 \mu\text{m} (20.602) \approx 20.602 \mu\text{m}$$

iii) low skewed nor2 gate ($k=\frac{2}{3}$)

$$W_p = 4 \mu\text{m} \left(\frac{2}{3}\right) (20.602) \approx 54.93863115 \mu\text{m} \approx 54.939 \mu\text{m}$$

$$W_n = 1 \mu\text{m} (20.602) \approx 20.602 \mu\text{m}$$

c) NAND2 gate sizing


$$Y = \overline{A \cdot B} \rightarrow \bar{Y} = \overline{(A \cdot B)}$$

$$Y = \overline{A} + \overline{B}$$



pmos

$$\bar{Y} = A \cdot B$$

nmos


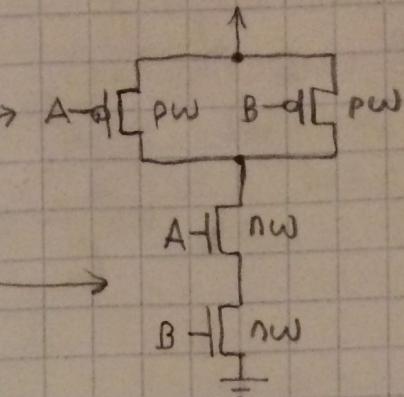


when $Y=1$, worst case delay is:

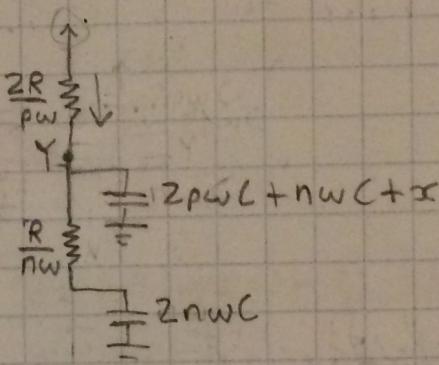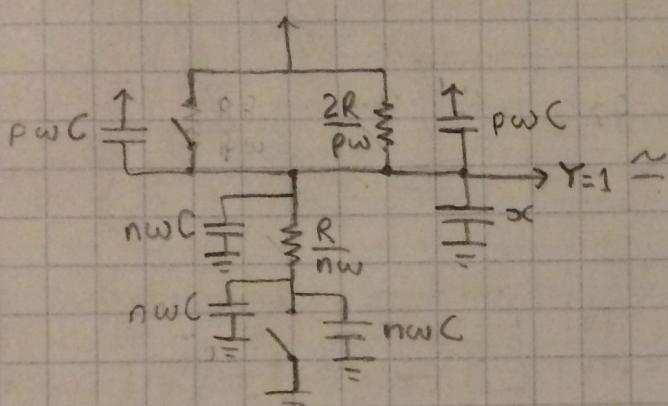

$$T_{pd़} = \frac{2R}{pw} (2pwC + nwC + x + 2nwC) = \frac{2R}{pw} (3nwC + 2pwC + x)$$

when $Y=0$, worst case delay is:

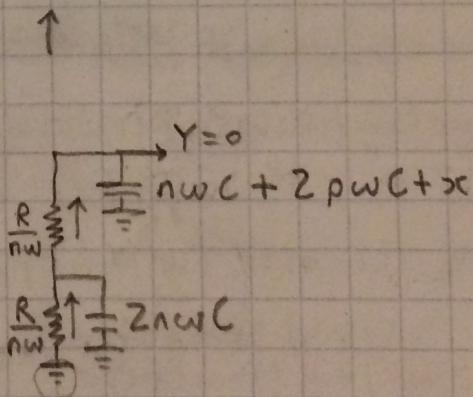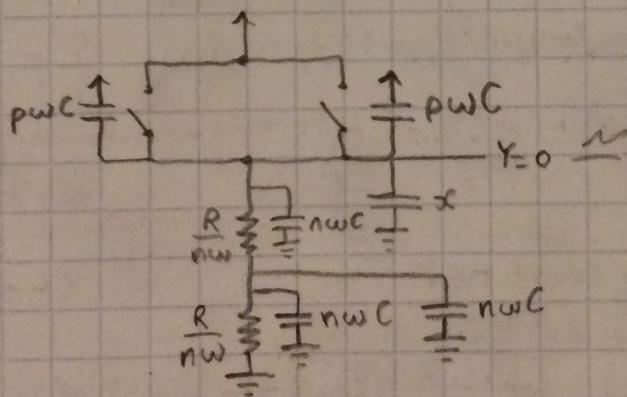

$$T_{pdf} = \frac{R}{nw} (2nwC + nwC + 2pwC + x) + \frac{R}{nw} (nwC + 2pwC + x)$$

$$= \frac{R}{nw} (4nwC + 4pwC + 2x) = \frac{2R}{nw} (2nwC + 2pwC + x)$$

$$T_{pdf} = K \cdot T_{pd़}$$

$$\frac{2R}{nw} (2nwC + 2pwC + x) = k \cdot \frac{2R}{pw} (3nwC + 2pwC + x)$$

The capacitances on each side don't cancel out! Approximate transistor sizing by assuming that resistances are more significant

$$\frac{2R}{nw} = k \cdot \frac{2R}{pw}$$

$$\frac{1}{n} = k \cdot \frac{1}{p}$$

$$\frac{p}{n} = \frac{k}{1} \xrightarrow{\text{assume } n=1\mu\text{m}} \frac{p}{1\mu\text{m}} = k$$

$$p = 1\mu\text{m} \cdot k$$

when $T_p = 100\text{ ps}$, assume:

unskewed gate ($k=1$)

load capacitance $x = 50\text{ fF}$

$$C = C_g x (\text{W}_n \text{ for unit nMOS}) = C_g x n = (18\text{ fF}/\mu\text{m})(1\mu\text{m}) = 1\text{ fF}$$

$$R = 10\text{ k}\Omega \cdot \ln(2)$$

$$n = 1\mu\text{m}$$

$$p = 1\mu\text{m} \cdot k = 1\mu\text{m}(1) = 1\mu\text{m}$$

$$T_p = T_{pdft} + T_{pdr} = \frac{2}{2} \left[\frac{2R}{nw} (2nwC + 2pwC + x) \right] + \left[\frac{2R}{pw} (3nwC + 2pwC + x) \right]$$

$$T_p = \frac{2R}{2w} \cdot \left[\frac{1}{n} (2nwC + 2pwC + x) + \frac{1}{p} (3nwC + 2pwC + x) \right]$$

$$\frac{T_p}{R} w = \left[2wC + 2\frac{p}{n}wC + \frac{x}{n} + 3\frac{n}{p}wC + 2wC + \frac{x}{p} \right]$$

$$= 4wC + \left(2\frac{p}{n} + 3\frac{n}{p} \right) wC + \left(\frac{1}{n} + \frac{1}{p} \right) x$$

$$= 4wC + \left(2\frac{(1)}{(1)} + 3\frac{(1)}{(1)} \right) wC + \left(\frac{1}{(1)} + \frac{1}{(1)} \right) x$$

$$= 4wC + 5wC + 2x \quad \rightarrow w = \frac{2x}{\frac{T_p}{R} - 9C} = \frac{2(50\text{ fF})}{\frac{100\text{ ps}}{10\text{ k}\Omega \cdot \ln(2)} - 9(1\text{ fF})}$$

$$\frac{T_p}{R} w = 9wC + 2x$$

$$\frac{T_p}{R} w - 9wC = 2x$$

$$w \left(\frac{T_p}{R} - 9C \right) = 2x$$

$$w = \frac{100}{\frac{10}{\ln(2)} - 9} = 18.42655496$$

$$w \approx 18.427$$

For all 3 circuits, $\text{W}_n = n \cdot w = (1\mu\text{m})(18.427) = 18.427\mu\text{m}$

i) high skewed circuit $\text{W}_p = (k=1.5)$

$$W_p = p \cdot w = (1\mu\text{m} \cdot k) \cdot w = 1\mu\text{m}(1.5)(18.427) = 27.63983245\mu\text{m} \approx 27.640\mu\text{m}$$

ii) unskewed circuit ($k=1$) W_p

$$W_p = p \cdot w = (1\mu\text{m} \cdot k) \cdot w = 1\mu\text{m}(1)(18.427) = 18.427\mu\text{m}$$

iii) low skewed circuit ($k=\frac{1}{1.5}$) W_p

$$W_p = p \cdot w = (1\mu\text{m} \cdot k) \cdot w = 1\mu\text{m}(\frac{1}{1.5})(18.427) = 12.28436998\mu\text{m} \approx 12.284\mu\text{m}$$


Q2. Rising, falling, average logic effort

a) NOR2 gates

$$\text{For nor 2: } w = 20.602 = w_{\text{nor}}$$

$$\text{For inverter: } w = 4.376 = w_{\text{inv}}$$
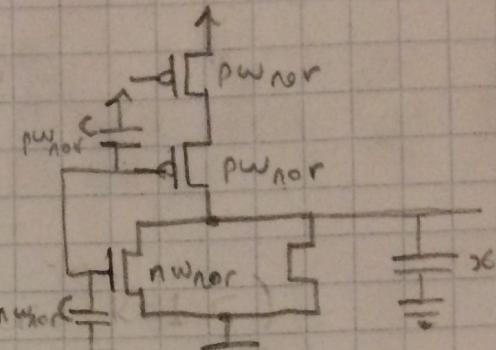
$$\frac{w_{\text{nor}}}{w_{\text{inv}}} = \frac{20.602}{4.376} \approx 4.708$$



$$h = \frac{\text{load cap}}{\text{nor input cap}} = \frac{x}{nW_{\text{nor}}C + pW_{\text{nor}}C} = \frac{x}{nW_{\text{nor}}C + 4knW_{\text{nor}}C}$$

$$\frac{P}{n} = \frac{4k}{1}, P = 4kn$$

$$\therefore h = \frac{xc}{nW_{\text{nor}}C(1+4k)} \text{ for Nor2}$$

t_{pd}' = Normalized delay of inverter: no load capacitance

$$t_{pd}' = t_{pd\text{f}} = t_{pd\text{r}} = \frac{R}{nW_{\text{inv}}} (nW_{\text{inv}}C + pW_{\text{inv}}C + x) \quad x=0$$

$$t_{pd}' = \frac{R}{nW_{\text{inv}}} (nW_{\text{inv}}C + (2kn)W_{\text{inv}}C + 0)$$

$$t_{pd}' = \frac{R}{nW_{\text{inv}}} \cdot (2k+1)nW_{\text{inv}}C = RC(2k+1) = t_{pd\text{r}}$$

i) NOR2 rising delay:

$$t_{pd\text{r}} = \frac{4R}{pW_{\text{nor}}} (2nW_{\text{nor}}C + 2pW_{\text{nor}}C + x) \quad \uparrow P = 4kn \leftarrow \frac{P}{n} = \frac{4k}{1}$$

$$= \frac{4R}{(4kn)W_{\text{nor}}} (2nW_{\text{nor}}C + 2(4kn)W_{\text{nor}}C + x)$$

$$t_{pd\text{r}} = \frac{R}{knW_{\text{nor}}} ((16k+2)nW_{\text{nor}}C + x)$$

$$t_{pd\text{r}} = 2\left(\frac{8k+1}{k}\right)RC + \frac{R}{k} \cdot \frac{xc}{nW_{\text{nor}}}$$

$$d_r = \frac{t_{pd\text{r}}}{t_{pd}'} = \frac{2\left(\frac{8k+1}{k}\right)RC + \frac{R}{k} \cdot \frac{xc}{nW_{\text{nor}}}}{RC(2k+1)}$$

$$d_r = 2\left(\frac{8k+1}{k(2k+1)}\right) + \frac{1}{k(2k+1)} \cdot \frac{x}{nW_{\text{nor}}C}$$

$$d_r = 2\left(\frac{8k+1}{k(2k+1)}\right) + \frac{(1+4k)}{k(2k+1)} \cdot \frac{x}{nW_{\text{nor}}C(1+4k)}$$

$$d_F = \frac{2}{k} \left(\frac{8k+1}{2k+1} \right) + \frac{(4k+1)}{k(2k+1)} \cdot h$$

Rising logic effort for NOR is: $g_r = \frac{4k+1}{k(2k+1)}$

$$\text{low skewed: } g_r = \frac{4\left(\frac{2}{3}\right)+1}{\left(\frac{2}{3}\right)\left(2\left(\frac{2}{3}\right)+1\right)} = \frac{\frac{8}{3}+\frac{3}{3}}{\left(\frac{2}{3}\right)\left(\frac{4}{3}+\frac{3}{3}\right)} = \frac{\left(\frac{11}{3}\right)}{\left(\frac{2}{3}\right)\left(\frac{7}{3}\right)} = \frac{11}{3} \cdot \frac{3}{2} \cdot \frac{3}{7} = \frac{33}{14}$$

$$\text{unskewed: } g_r = \frac{4(1)+1}{(1)(2(1)+1)} = \frac{4+1}{2+1} = \frac{5}{3}$$

$$\text{high skewed: } g_r = \frac{4\left(\frac{3}{2}\right)+1}{\left(\frac{3}{2}\right)\left(2\left(\frac{3}{2}\right)+1\right)} = \frac{6+1}{\frac{3}{2}(3+1)} = \frac{7}{\frac{3}{2}(4)} = \frac{7}{6}$$

(ii) NOR2 falling delay:

$$t_{pdF} = \frac{R}{nw} (2nwC + 3pwC + x) = \frac{R}{nw} (2nwC + 3(4kn)wC + x) \\ \frac{R}{n} = \frac{4k}{1} \rightarrow p = 4kn$$

$$t_{pdF} = \frac{R}{nw} (2nwC + 12knwC + x) = 2RC + 12kRC + \frac{Rx}{nw}$$

$$t_{pdF} = 2RC(1+6k) + \frac{Rx}{nw}$$

$$df = \frac{t_{pdF}}{t_{pd'}} = \frac{2RC(1+6k) + \frac{Rx}{nw}}{RC(2k+1)} = 2\left(\frac{6k+1}{2k+1}\right) + \frac{x}{nwC(2k+1)}$$

$$df = 2\left(\frac{6k+1}{2k+1}\right) + \underbrace{\frac{(4k+1)}{(2k+1)}}_{\frac{4k+1}{2k+1}} \cdot \underbrace{\frac{x}{nwC(4k+1)}}_{\frac{4k+1}{2k+1}}$$

Falling logic effort for NOR is: $g_f = \frac{4k+1}{2k+1}$

$$\text{low skewed: } g_f = \frac{4\left(\frac{2}{3}\right)+1}{2\left(\frac{2}{3}\right)+1} = \frac{\frac{8}{3}+\frac{3}{3}}{\frac{4}{3}+\frac{3}{3}} = \frac{\left(\frac{11}{3}\right)}{\left(\frac{7}{3}\right)} = \frac{11}{3} \cdot \frac{3}{7} = \frac{11}{7}$$

$$\text{unskewed: } g_f = \frac{4(1)+1}{2(1)+1} = \frac{4+1}{2+1} = \frac{5}{3}$$

$$\text{high skewed: } g_f = \frac{4\left(\frac{3}{2}\right)+1}{2\left(\frac{3}{2}\right)+1} = \frac{6+1}{3+1} = \frac{7}{4}$$

(iii) NOR2 average delay:

$$t_p = \frac{t_{pdF} + t_{pdR}}{2} \rightarrow d_{avg} = \frac{t_p}{t_{pd'}} = \frac{\left(\frac{t_{pdF} + t_{pdR}}{2}\right)}{t_{pd'}} = \frac{1}{2} \left(\frac{t_{pdF} + t_{pdR}}{t_{pd'}} \right)$$

$$d_{avg} = \frac{\left(\frac{t_{pdF}}{t_{pd'}} + \frac{t_{pdR}}{t_{pd'}}\right)}{2} = \frac{df + dr}{2} = \frac{p_f + g_f h + p_r + g_r h}{2}$$

$$d_{avg} = \frac{p_f + p_r}{2} + \frac{(g_f + g_r) \cdot h}{2} \rightarrow \therefore g_{avg} = \frac{g_f + g_r}{2}$$

$$\text{low skewed: } g_{avg} = \frac{\left(\frac{11}{7}\right) + \left(\frac{33}{14}\right)}{2} = \frac{\frac{22}{14} + \frac{33}{14}}{2} = \frac{\frac{55}{14}}{2} = \frac{55}{28}$$

$$\text{unskewed: } g_{avg} = \frac{\left(\frac{5}{3}\right) + \left(\frac{5}{3}\right)}{2} = \frac{5}{3}$$

$$\text{high skewed: } g_{avg} = \frac{\left(\frac{7}{4}\right) + \left(\frac{7}{6}\right)}{2} = \frac{7}{2} \left(\frac{1}{3} + \frac{1}{2} \right) = \frac{7}{4} \left(\frac{2}{6} + \frac{3}{6} \right) = \frac{7}{4} \left(\frac{5}{6} \right) = \frac{35}{24}$$

b) NAND2 gates:

$$h = \frac{\text{load cap}}{\text{input cap}} = \frac{x}{nwC + pwC} = \frac{x}{nwC + (kn)wC} = \frac{x}{nwC(k+1)}$$

$$\frac{P}{n} = \frac{K}{1} \rightarrow P = kn$$

i) NAND2 rising delay:

$$t_{pdR} = \frac{2R}{pw} (3nwC + 2pwC + x) = \frac{2R}{(kn)w} (3nwC + 2(kn)wC + x)$$

$$t_{pdR} = \frac{2R}{knw} ((3+2k)nwC + x) = 2RC \left(\frac{3+2k}{k} \right) + \frac{2Rx}{knw}$$

$$d_r = \frac{t_{pdR}}{t_{pd'}} = \frac{2RC \left(\frac{3+2k}{k} \right) + \frac{2Rx}{knw}}{RC(2k+1)} = \frac{2}{k} \left(\frac{3+2k}{1+2k} \right) + \frac{2x}{nwC}$$

$$d_r = \frac{2}{k} \left(\frac{2k+3}{2k+1} \right) + 2(k+1) \cdot \frac{x}{nwC(k+1)} \leftarrow h$$

rising logic effort for NAND2: $g_r = 2(k+1)$

$$\text{low skewed: } g_r = 2 \left(\left(\frac{2}{3} \right) + 1 \right) = 2 \left(\frac{2}{3} + \frac{3}{3} \right) = 2 \left(\frac{5}{3} \right) = \frac{10}{3}$$

$$\text{unskewed: } g_r = 2((1)+1) = 2(2) = 4$$

$$\text{high skewed: } g_r = 2 \left(\left(\frac{3}{2} \right) + 1 \right) = 2 \left(\frac{3}{2} + \frac{2}{2} \right) = 2 \left(\frac{5}{2} \right) = 5$$

ii) NAND2 falling delay:

$$t_{pdf} = \frac{2R}{nw} (2nwC + 2pwC + x) = \frac{2R}{nw} (2nwC + 2(kn)wC + x)$$

$$t_{pdf} = \frac{2R}{nw} (2(1+k)nwC + x) = 4RC(1+k) + \frac{2Rx}{nw}$$

$$d_f = \frac{t_{pdf}}{t_{pd'}} = \frac{4RC(1+k) + \frac{2Rx}{nw}}{RC(2k+1)} = 4 \left(\frac{1+k}{2k+1} \right) + \frac{2x}{nwC(2k+1)}$$

$$d_f = 4 \left(\frac{k+1}{2k+1} \right) + 2 \left(\frac{k+1}{2k+1} \right) \cdot \frac{x}{nwC(k+1)} \leftarrow h$$

$$\text{falling logic effort for NAND2: } g_f = 2 \frac{(k+1)}{(2k+1)}$$

$$\text{low skewed: } g_f = 2 \frac{\left(\frac{2}{3} + 1\right)}{\left(2\left(\frac{2}{3}\right) + 1\right)} = 2 \frac{\left(\frac{2}{3} + \frac{3}{3}\right)}{\left(\frac{4}{3} + \frac{3}{3}\right)} = 2 \frac{\left(\frac{5}{3}\right)}{\left(\frac{7}{3}\right)} = 2 \left(\frac{5}{7}\right) \left(\frac{2}{3}\right)$$

\downarrow

$g_f = \frac{10}{7}$

$$\text{unskewed: } g_f = 2 \frac{\left(\frac{1}{2} + 1\right)}{\left(2\left(\frac{1}{2}\right) + 1\right)} = 2 \frac{\left(\frac{1}{2} + 1\right)}{\left(2 + 1\right)} = 2 \left(\frac{2}{3}\right) = \frac{4}{3}$$

$$\text{high skewed: } g_f = 2 \frac{\left(\frac{3}{2} + 1\right)}{\left(2\left(\frac{3}{2}\right) + 1\right)} = 2 \frac{\left(\frac{3}{2} + \frac{2}{2}\right)}{\left(3 + 1\right)} = 2 \frac{\left(\frac{5}{2}\right)}{4} = \frac{5}{4}$$

(iii) NAND2 average logic effort

$$g_{avg} = \frac{g_f + g_r}{2} = \frac{1}{2}(g_f + g_r)$$

$$\text{low skewed: } g_{avg} = \frac{1}{2} \left[\left(\frac{10}{7} \right) + \left(\frac{10}{3} \right) \right] = \frac{10}{2} \left(\frac{1}{7} + \frac{1}{3} \right) = 5 \left(\frac{3}{21} + \frac{7}{21} \right)$$

$$g_{avg} = 5 \left(\frac{10}{21} \right) = \frac{50}{21}$$

$$\text{unskewed: } g_{avg} = \frac{1}{2} \left(\left(4 \right) + \left(\frac{4}{3} \right) \right) = \frac{1}{2} \left(\frac{12}{3} + \frac{4}{3} \right) = \frac{1}{2} \left(\frac{16}{3} \right) = \frac{8}{3}$$

$$\text{high skewed: } g_{avg} = \frac{1}{2} \left(\left(5 \right) + \left(\frac{5}{4} \right) \right) = \frac{1}{2} \left(\frac{20}{4} + \frac{5}{4} \right) = \frac{1}{2} \left(\frac{25}{4} \right) = \frac{25}{8}$$